

Problem ①

2 wire topology

$l \triangleq$ length of line = 4,260 km

$a \triangleq$ radius of each line = 1 cm

$d \triangleq$ spacing between the two lines = 5 cm

a) From Iran & Iran, table 2.2, page 85:

$$L' = 0.4 \ln \left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a}\right)^2 - 1} \right] \mu\text{H/m}$$

$$d = 5 \text{ cm}$$

$$a = 1 \text{ cm}$$

$$\Rightarrow L' = 0.627 \mu\text{H/m}$$

$$L = L' \cdot l$$

$$= 0.627 \mu\text{H/m} \cdot 4,260 \text{ km}$$

$$\Rightarrow \boxed{L = 2.67 \text{ H}}$$

b) Let $R \triangleq$ resistance of each wire at DC

$$R = \frac{\rho \cdot l}{A}$$

$$\rho_{\text{copper}} = 1.7 \times 10^{-8} \Omega \cdot \text{m}$$

$$A = \pi a^2, \quad a = 1 \text{ cm} \Rightarrow A = \pi \cdot 10^{-4} \text{ m}^2$$

$$l = 4,260 \text{ km}$$

$$\Rightarrow \boxed{R = 230 \Omega}$$

c) From I_{nan} & I_{nan} , table 2.2, page 85:

$$C' = \frac{27.8}{\ln \left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a} \right)^2 - 1} \right]}$$

$$d = 5 \text{ cm}$$

$$a = 1 \text{ cm}$$

$$\Rightarrow C' = 17.74 \text{ pF/m}$$

$$C = C' \cdot l$$

$$= 17.74 \text{ pF/m} \times 4,260 \text{ km}$$

$$\Rightarrow \boxed{C = 75.6 \text{ } \mu\text{F}}$$

d) let $t_p \triangleq$ propagation delay along the line.

$$t_p = \frac{l}{v}$$

if the line is in air,

$$v = 3 \times 10^8 \text{ m/s}$$

$$\Rightarrow t_p = \frac{4,260 \times 10^3 \text{ m}}{3 \times 10^8 \text{ m/s}}$$

$$\Rightarrow \boxed{t_p = 14.2 \text{ ns}}$$

e) Increasing the voltage between the two lines increases the E field in the dielectric. If the E field increases beyond a critical value E_{crit} , the dielectric breaks down resulting in large dielectric current and the transmission line becomes dysfunctional.


Assuming the dielectric is Teflon,

$$E_{crit, \text{Teflon}} = 60 \frac{\text{MV}}{\text{m}}$$

$$\begin{aligned} V_{max} &= E_{crit} \times d \\ &= 60 \frac{\text{MV}}{\text{m}} \times 5 \text{ cm} \end{aligned}$$

$$\Rightarrow \boxed{V_{max} = 3 \text{ MV}}$$

g) simple LR circuit

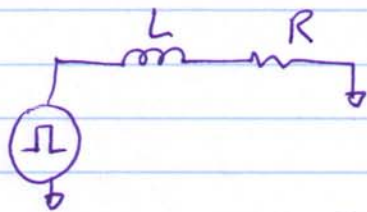

from (a) : $L = 2.67 \text{ H}$

from (b) : $R = 2 \times 230 \Omega = 460 \Omega$ (each wire has resistance of 230Ω)

let $\tau \triangleq$ circuit time constant

$$\Rightarrow \tau = \frac{L}{R}$$

$$= \frac{2.67 \text{ H}}{460 \Omega}$$

$$\Rightarrow \tau = 5.72 \text{ ms}$$

let $t_r \triangleq$ rise time


$$t_r \approx 5 \tau$$

$$\Rightarrow \boxed{t_r \approx 28.6 \text{ ms}}$$

The pulse contains many high frequency components.

Since $\lambda = \frac{c}{f}$, $l \gg \lambda$ for the high frequency components.

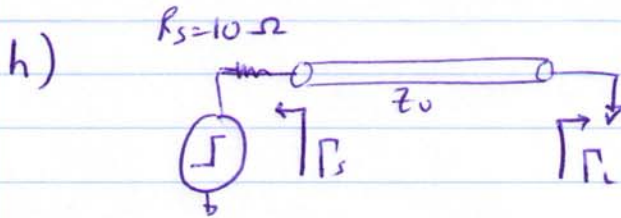In this case, the line exhibits distributed effects and should be modeled as a transmission line. LR circuits do not model reflection or wave phenomena.




$$Z_0 = \sqrt{\frac{L'}{C'}} = \sqrt{\frac{0.627 \text{ nH/m}}{17.74 \text{ pF/m}}}$$

$$\Rightarrow Z_0 = 188 \Omega$$


$$\Gamma_L = \frac{0 - Z_0}{0 + Z_0} \Rightarrow \Gamma_L = -1$$
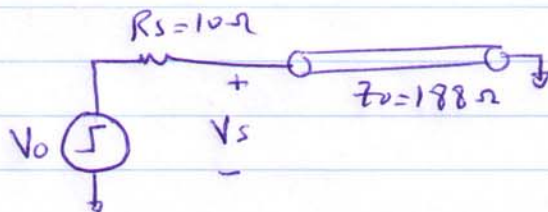
$$\Gamma_s = \frac{R_s - Z_0}{R_s + Z_0} = \frac{10 - 188}{10 + 188} \Rightarrow \Gamma_s = -0.9$$



$$@ t=0: V_s = V_1^+ = \frac{Z_0}{R_s + Z_0} \cdot V_0 = \frac{188}{10 + 188} V_0 = 0.95 V_0$$

bounce diagram V_1^+

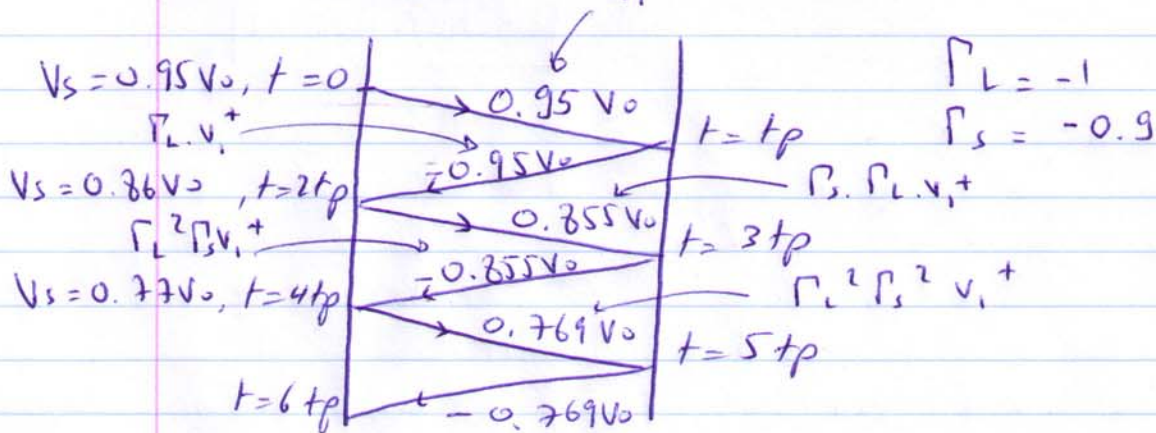

$$V_s|_{t=0} = 0.95 V_0$$

$$V_s|_{t=\infty} = 0$$

We need to find when V_s becomes $0.1 \times V_s|_{t=0}$

From the bounce diagram, we can deduce that:

$$V_s|_{t=2nt_p} = (\Gamma_L \Gamma_s)^n \cdot V_s|_{t=0}, \quad n > 1$$

$$\text{we need } V_s = 0.1 V_s|_{t=0}$$

\Rightarrow solve for n , replacing $V_s|_{t=2nt_p}$ by $0.1 V_s|_{t=0}$

$$\Rightarrow 0.1 V_s|_{t=0} = (\Gamma_L \Gamma_s)^n V_s|_{t=0}$$

$$\Rightarrow 0.1 = (0.9)^n$$

$$\Rightarrow \log_{0.9}(0.1) = \log_{0.9}(0.9^n) = n \cdot \log_{0.9}(0.9) = n$$

$$\Rightarrow n = \log_{0.9}(0.1)$$

$$\Rightarrow n = 22$$


V_s of $0.1 V_s|_{t=0}$ occurs @ $t = 2n t_p$

$t_p = 14.2 \text{ ms}$ (from (d))

$$\Rightarrow \boxed{t = 624.8 \text{ ms}}$$

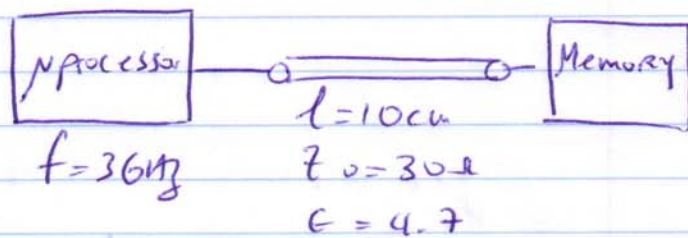Problem (6)

$$\begin{aligned} f &= 3 \text{ GHz} \\ l &= 10 \text{ cm} \\ \epsilon &= 4.7 \\ Z_0 &= 30 \Omega \end{aligned}$$



$$v = \frac{c}{\sqrt{\epsilon_r \mu_r}} = \frac{3 \times 10^8 \text{ m/s}}{\sqrt{4.7 \times 1}}$$

$$\Rightarrow v = 1.38 \times 10^8 \text{ m/s}$$

To read data from the memory, the signal has to propagate from the processor to the memory and back from the memory to the processor.

$$\Rightarrow \text{it takes } 2 \times \frac{l}{v} = 2 \times \frac{10 \text{ cm}}{1.38 \times 10^8 \text{ m/s}} = 1.45 \text{ ns}$$

$$\text{clock cycle} = \frac{1}{f} = \frac{1}{3 \times 10^9 \text{ s}} = \frac{1}{3} \text{ ns}$$

$$\Rightarrow \text{number of cycles to read data} = \frac{1.45 \text{ ns}}{\frac{1}{3} \text{ ns}} = \boxed{4.35 \text{ cycles}}$$

It is recommended to terminate the line at both ends with an impedance equal to $Z_0 = 30 \Omega$. This stops reflections at both ends resulting in faster steady state convergence.