

1. Suppose the resonant frequency  $\omega_0$  is equal to  $(LC)^{-0.5}$ . The load impedance  $Z_L$  is

$$Z_L = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

If  $\omega = \omega_0 + \Delta\omega$ ,  $Z_L$  is equal to

$$\begin{aligned} Z_L &= R + j(\omega_0 + \Delta\omega)L + \frac{1}{j(\omega_0 + \Delta\omega)C} = R + j\left[\omega_0 L\left(1 + \frac{\Delta\omega}{\omega_0}\right) - \frac{1}{\omega_0\left(1 + \frac{\Delta\omega}{\omega_0}\right)C}\right] \\ &\approx R + j\left[\omega_0 L\left(1 + \frac{\Delta\omega}{\omega_0}\right) - \frac{1}{\omega_0 C}\left(1 - \frac{\Delta\omega}{\omega_0}\right)\right] = R + j\left[\Delta\omega L + \frac{\Delta\omega}{\omega_0^2 C}\right] \end{aligned}$$

The last equality holds because  $\omega_0 = (LC)^{-0.5}$ . Furthermore,

$$R + j\left[\Delta\omega L + \frac{\Delta\omega}{\omega_0^2 C}\right] = R + j\frac{\Delta\omega}{\omega_0}\left[\omega_0 L + \frac{1}{\omega_0 C}\right] = R + j\frac{\Delta\omega}{\omega_0}(2\omega_0 L) = R + j2\Delta\omega L$$

Using the values of the inductance and capacitance, the length of 2 cm corresponds  $1.5\pi$ .

$$\beta_0 l = \frac{\omega_0}{v} l = \frac{1}{v\sqrt{LC}} l = \frac{2cm}{10^8 m/s \sqrt{2 \times 10^{-9} \times 9.01 \times 10^{-13}}} = 1.5\pi$$

In general,  $\beta l = (\beta_0 + \Delta\beta)l = \frac{\omega_0 + \Delta\omega}{v} l = \beta_0 l \left(1 + \frac{\Delta\omega}{\omega_0}\right)$ . Thus  $Z_{in}$  is

$$\begin{aligned} Z_{in} &= Z_0 \frac{R + j2\Delta\omega L + jZ_0 \tan(1.5\pi(1 + \Delta\omega/\omega_0))}{Z_0 + j(R + j2\Delta\omega L)\tan(1.5\pi(1 + \Delta\omega/\omega_0))} \approx Z_0 \frac{jZ_0 \tan(1.5\pi(1 + \Delta\omega/\omega_0))}{j(R + j2\Delta\omega L)\tan(1.5\pi(1 + \Delta\omega/\omega_0))} \\ &= \frac{Z_0^2}{(R + j2\Delta\omega L)} \end{aligned}$$

The approximation holds because  $\tan(1.5\pi(1 + \Delta\omega/\omega_0)) \gg R, \Delta\omega L, Z_0$ . This expression has the same form as a parallel RLC circuit, with

$$R_{eq} = \frac{Z_0^2}{R}, \quad C_{eq} = \frac{L}{Z_0^2}, \quad L_{eq} = \frac{1}{\omega_0^2 \frac{L}{Z_0^2}} = Z_0^2 C$$

Therefore, the input impedance  $Z_{in}$  is that of a second order circuit. Also,  $L_{eq}C_{eq} = LC = \omega_0^{-2}$ , so our assumption is correct, i.e.,  $\omega_0 = (LC)^{-0.5}$ . The Q factor is

$$Q = \omega_0 R_{eq} C_{eq} = \frac{L/R}{\sqrt{LC}} = \sqrt{\frac{L}{C}} R = 94$$

The equivalent circuit is  $L_{eq} = Z_0^2 C = 5 \mu F$ ,  $C_{eq} = L/Z_0^2 = 0.3604 \text{ fH}$ , and  $R_{eq} = Z_0^2/R = 1250$  in parallel.

2. For a lossy line, the input impedance has a form

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tanh(\alpha l + j\beta l)}{Z_0 + jZ_L \tanh(\alpha l + j\beta l)}$$

where  $Z_L = 2j\Delta\omega L$ . Also,

$$\tanh(\alpha l + j\beta l) = \frac{\sinh(2\alpha l)}{\cosh(2\beta l) + \cosh(2\alpha l)} + j \frac{\sin(2\beta l)}{\cos(2\beta l) + \cosh(2\alpha l)}$$

$\sin(2\beta l) = \sin(3\pi(1 + \Delta\omega/\omega_0)) \approx \sin(3\pi) + \cos(3\pi) * (3\pi\Delta\omega/\omega_0) = -3\pi\Delta\omega/\omega_0$ . Likewise,  $\cos(2\beta l) \approx \cos(3\pi) - \sin(3\pi) * (3\pi\Delta\omega/\omega_0) = -1$ . So,

$$\tanh(\alpha l + j\beta l) = \frac{\sinh(2\alpha l)}{\cosh(2\alpha l) - 1} - j \frac{3\pi\Delta\omega/\omega_0}{\cosh(2\alpha l) - 1}$$

The input impedance is then equal to

$$\begin{aligned} Z_{in} &= Z_0 \frac{2j\Delta\omega L + jZ_0 \left( \frac{\sinh(2\alpha l)}{\cosh(2\alpha l) - 1} - j \frac{3\pi\Delta\omega/\omega_0}{\cosh(2\alpha l) - 1} \right)}{Z_0 + j2j\Delta\omega L \left( \frac{\sinh(2\alpha l)}{\cosh(2\alpha l) - 1} - j \frac{3\pi\Delta\omega/\omega_0}{\cosh(2\alpha l) - 1} \right)} \\ &= Z_0 \frac{Z_0 \frac{3\pi\Delta\omega/\omega_0}{\cosh(2\alpha l) - 1} + j \left( 2\Delta\omega L + Z_0 \frac{\sinh(2\alpha l)}{\cosh(2\alpha l) - 1} \right)}{Z_0 - 2\Delta\omega L \frac{\sinh(2\alpha l)}{\cosh(2\alpha l) - 1} + j2\Delta\omega L \frac{3\pi\Delta\omega/\omega_0}{\cosh(2\alpha l) - 1}} \\ &\approx Z_0 \frac{Z_0 3\pi\Delta\omega/\omega_0 + j(2\Delta\omega L(\cosh(2\alpha l) - 1) + Z_0 \sinh(2\alpha l))}{Z_0 (\cosh(2\alpha l) - 1) - 2\Delta\omega L \sinh(2\alpha l)} \end{aligned}$$

The third term in the denominator has  $\Delta\omega^2$  dependence and is thus negligible.

**3-31. Quarter-wave matching.** (a) For the first circuit with the single quarter-wave transformer, we find

$$Z_0 = \sqrt{Z_0 R_L} = \sqrt{(50)(400)} \simeq 141.4\Omega$$

For the second circuit involving two quarter-wave sections cascaded together, the input impedance of the two transformers can be written as

$$Z_{in2} = \frac{Z_{Q2}^2}{R_L} \quad \text{and}$$

$$Z_{in1} = \frac{Z_{Q1}^2}{Z_{in2}} = \frac{Z_{Q1}^2}{Z_{Q2}^2} R_L = Z_0$$

resulting in  $Z_{Q1}/Z_{Q2} = \sqrt{Z_0/R_L}$ . But it is also given that  $Z_{Q1}Z_{Q2} = Z_0R_L$ . Therefore, solving these two equations simultaneously, we have

$$Z_{Q1}^2 = \sqrt{\frac{Z_0}{R_L}} (Z_0 R_L) = \sqrt{Z_0^3 R_L} = \sqrt{(50)^3 (400)}$$

yielding  $Z_{Q1} \simeq 84.1\Omega$  and

$$Z_{Q2} = \frac{Z_0 R_L}{Z_{Q1}} \simeq \frac{(50)(400)}{84.1} \simeq 238\Omega$$

respectively.

(b) At 15% above the design frequency we have for the first circuit:

$$Z_{in} = Z_Q \frac{R_L + jZ_Q \tan[(2\pi)(1/4)(1.15)]}{Z_Q + jR_L \tan[(2\pi)(1/4)(1.15)]} \simeq 60.21e^{j29.33^\circ}$$

and

$$|\Gamma_{in}| = \left| \frac{Z_{in} - 50}{Z_{in} + 50} \right| \simeq 0.278 \quad \rightarrow \quad S = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|} \simeq 1.768$$

and for the second circuit we have

$$Z_{in} = Z_{Q1} \frac{Z'_{in} + jZ_{Q1} \tan[(2\pi)(1/4)(1.15)]}{Z_{Q1} + jZ'_{in} \tan[(2\pi)(1/4)(1.15)]}$$

where


$$Z'_{in} = Z_{Q2} \frac{R_L + jZ_{Q2} \tan[(2\pi)(1/4)(1.15)]}{Z_{Q2} + jR_L \tan[(2\pi)(1/4)(1.15)]}$$

substituting values we find  $Z_{in} \simeq 44.55e^{j3.98^\circ}$  and

$$|\Gamma_{in}| = \left| \frac{Z_{in} - 50}{Z_{in} + 50} \right| \simeq 0.0673 \quad \rightarrow \quad S = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|} \simeq 1.144$$

Similar analysis for 15% below the design frequency gives  $S \simeq 1.22$  for the first circuit and  $S \simeq 1.02$  for the second circuit.

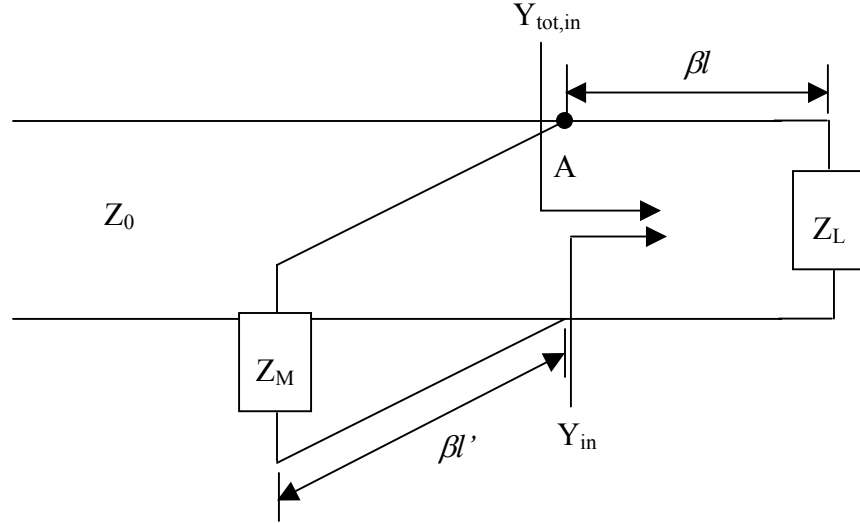4. This problem is similar to the example 3-16 in the textbook. For matching of the load with either a short or an open shunt stub, we have the following circuit:



Where  $Z_M$  is either 0 or infinity for a short or an open stub, respectively.

Since we are dealing with shunt stub, admittance would simplify the calculation. The equivalent admittance at point A (excluding the stub for a moment) is given by

$$Y_{in} = Y_0 \frac{Y_L + jY_0 \tan(\beta l)}{Y_0 + jY_L \tan(\beta l)}$$

where  $Y_0 = [Z_0]^{-1} = 1/50$ , and  $Y_L = [Z_L]^{-1} = 1/100 + j3/100$ .

Separating the expression into the real and imaginary parts gives

$$Y_{in} = \frac{1 + x^2}{(10 + 15x)^2 + 25x^2} + j \frac{3x^2 - 3x - 3}{(10 + 15x)^2 + 25x^2}$$

where  $x = \tan(\beta l)$ .

Since a short or an open stub can behave as a purely reactive element, the real part of  $Y_{in}$  above should be equal to  $Y_0$  in order for the matching to take place. Thus, we have,

$$\frac{1 + x^2}{(10 + 15x)^2 + 25x^2} = Y_0 = \frac{1}{50}$$

The solution of this equation is:  $\tan(\beta l) = \frac{-3-\sqrt{5}}{4}$  or  $\frac{-3+\sqrt{5}}{4}$ . Both of them are negative. This means that  $\beta l$  is larger than  $\pi/2$ . The more negative value represents a point closer to the load and this value will be used in the following calculation.

$$\tan(\beta l) = \frac{-3-\sqrt{5}}{4} \Leftrightarrow \beta l = 2.22315.$$

Substitute this value into the imaginary part of  $Y_{in}$  and get

$$j \frac{3x^2 - 3x - 3}{(10 + 15x)^2 + 25x^2} \Big|_{x=\frac{-3-\sqrt{5}}{4}} = 0.044721 j$$

The stub needs to have an impedance opposite to the value above in order to cancel the reactive part of the  $Y_{in}$  for matching. For a short stub,  $Y = -jY_0 \cot(\beta l')$ . Therefore, we want

$$\frac{0.044721}{Y_0} = \cot(\beta l') \Leftrightarrow \beta l' = 0.420534.$$

The input impedance at point A including the stub is

$$Y_{tot,in} = \frac{1 + \tan^2(2.22315)}{(10 + 15 \tan(2.22315))^2 + 25 \tan^2(2.22315)} + j \left( \frac{3 \tan^2(2.22315) - 3 \tan(2.22315) - 3}{(10 + 15 \tan(2.22315))^2 + 25 \tan^2(2.22315)} - \frac{Y_0}{\tan(0.420534)} \right)$$

The imaginary part is equal to zero. The SWR is given by

$$S = \frac{1 + \left| \frac{Y_0 - Y_{in}}{Y_0 + Y_{in}} \right|}{1 - \left| \frac{Y_0 - Y_{in}}{Y_0 + Y_{in}} \right|}$$


In general, for  $\beta' \neq \beta$ , i.e.,  $\beta' l = \beta l * n$ , where  $n$  is the ratio of  $\beta'$  to  $\beta$ , the input impedance shown above is

$$Y_{tot,in}(n) = \frac{1 + \tan^2(2.22315n)}{(10 + 15 \tan(2.22315n))^2 + 25 \tan^2(2.22315n)} + j \left( \frac{3 \tan^2(2.22315n) - 3 \tan(2.22315n) - 3}{(10 + 15 \tan(2.22315n))^2 + 25 \tan^2(2.22315n)} - \frac{Y_0}{\tan(0.420534 * n)} \right)$$

and the SWR is equal to

$$S = \frac{1 + \left| \frac{Y_0 - Y_{in}(n)}{Y_0 + Y_{in}(n)} \right|}{1 - \left| \frac{Y_0 - Y_{in}(n)}{Y_0 + Y_{in}(n)} \right|}$$

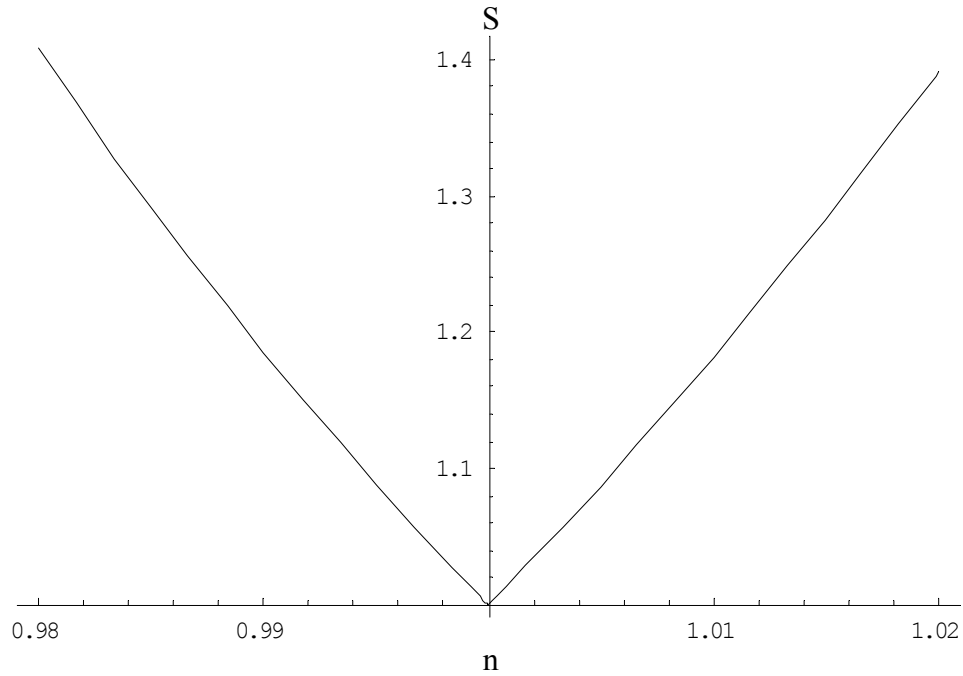SWR can be plotted as a function of n, representing the amount of shift in the signal frequency / phase constant from the ones used in calculating the numbers above.




The values of n where S = 1.2 are 0.989 and 1.01, for a short stub.

Following the same procedure, we have these for an open stub

$$Y = jY_0 \tan(\beta l') \Leftrightarrow \frac{0.044721}{Y_0} = -\tan(\beta l') \Leftrightarrow \beta l' = 1.99133.$$


$$Y_{tot,in}(n) = \frac{1 + \tan^2(2.22315n)}{(10 + 15 \tan(2.22315n))^2 + 25 \tan^2(2.22315n)} + j \left( \frac{3 \tan^2(2.22315n) - 3 \tan(2.22315n) - 3}{(10 + 15 \tan(2.22315n))^2 + 25 \tan^2(2.22315n)} - Y_0 \tan(1.99133 * n) \right)$$

The plot of S vs. n:

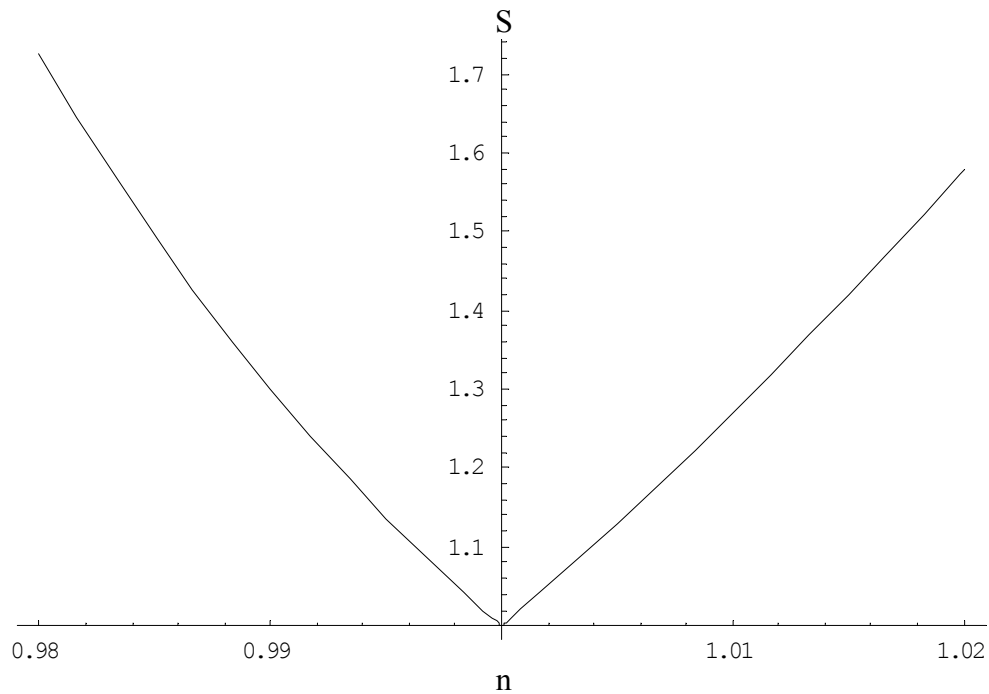

The values of n where S = 1.2 are 0.993 and 1.01.

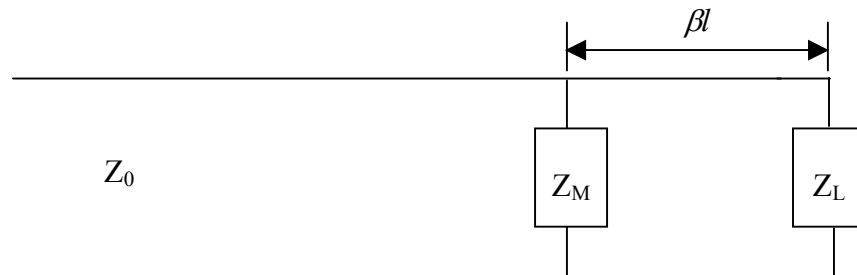For impedance matching with a lumped element, we have the following circuit:



To keep the problem simple, let's make the lumped element  $Z_M$  a purely reactive component. With this constraint, the real part of  $Y_{in}$  needs to match the characteristic impedance of the transmission line, just like the cases of short and open stubs above. The

previous calculation gives  $\beta l = 2.22315$  or  $2.95288$ . Just as before, we pick the shortest distance  $\beta l = 2.22315$ . At this length,  $Y_{in}$  is equal to

$$Y_{in} = 0.02 + 0.0447214j$$

The positive imaginary part implies that the lumped element needs to be an inductor in order to make the impedance matching work. So,


$$Y_M = 1/Z_M = -j/(\omega L) = -j/(\beta v L) = -0.0447214j$$

where  $v$  is the propagation velocity of the transmission line. The velocity is property of the transmission line, and does not depend on the signal frequency.

In general,  $Y_{tot,in}$  is

$$Y_{tot,in}(n) = \frac{1 + \tan^2(2.22315n)}{(10 + 15 \tan(2.22315n))^2 + 25 \tan^2(2.22315n)} + j \left( \frac{3 \tan^2(2.22315n) - 3 \tan(2.22315n) - 3}{(10 + 15 \tan(2.22315n))^2 + 25 \tan^2(2.22315n)} - \frac{0.04427214}{n} \right)$$

The plot of S vs. n:

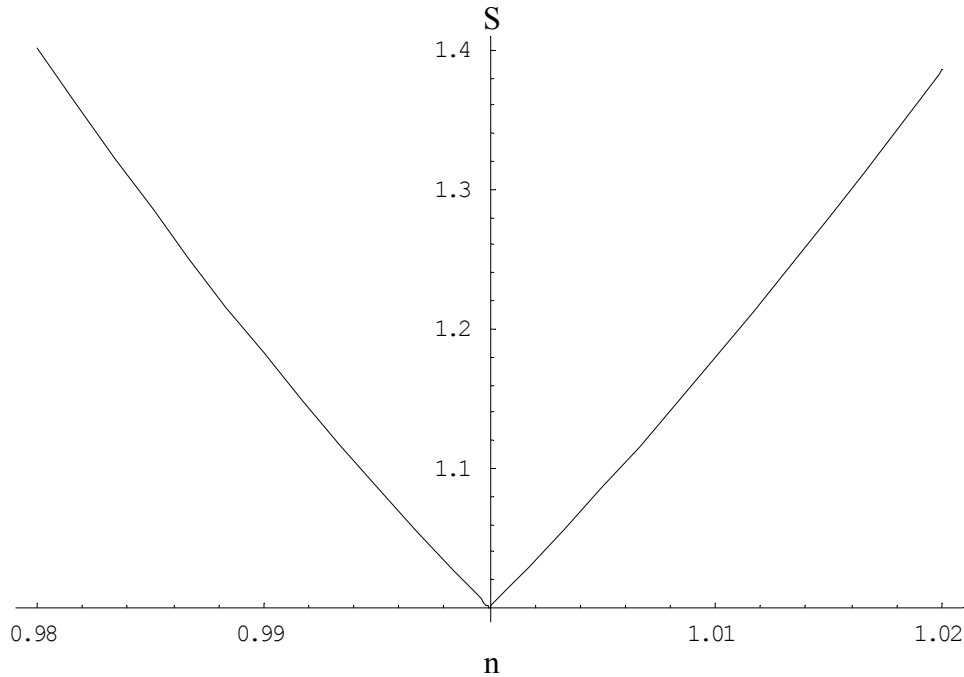

The values of  $n$  where  $S = 1.2$  are 0.989 and 1.01.



In summary,

	Bandwidth for $S \leq 1.2$
Short	$0.989 \omega_0$ to $1.01 \omega_0$
Open	$0.993 \omega_0$ to $1.01 \omega_0$
Lumped	$0.989 \omega_0$ to $1.01 \omega_0$

- 3-38. **Quarter-wave matching.** (a) We start by writing the input impedance of the  $50\Omega$  transmission line of length  $l$  on the right looking toward the load  $Z_L = 40 + j30 \Omega$  as

$$\begin{aligned} Z_1 &= (50) \frac{(40 + j30) + j50T}{50 + j(40 + j30)T} = (50) \frac{40 + j(30 + 50T)}{(50 - 30T) + j40T} \\ &= (50) \frac{[40 + j(30 + 50T)][(50 - 30T) - j40T]}{(50 - 30T)^2 + (40T)^2} \end{aligned}$$

where  $T = \tan(\beta l)$  and  $\beta = 2\pi/\lambda$ . Note that the input impedance of the  $50\Omega$  line at the location of the quarter-wave transformer must be purely real so that a match can be achieved. Therefore, to find the location of the quarter-wave transformer with respect to the load, we equate the imaginary part of  $Z_1$  to zero, i.e.,

$$\Im\{Z_1\} = 0 \quad \rightarrow \quad (30 + 50T)(50 - 30T) - (40)^2 T = 0$$

$$\rightarrow 15T^2 = 15 \quad \rightarrow \quad T = \tan(\beta l) = \pm 1$$

From  $\tan(\beta l) = +1$ , we find  $l/\lambda = 0.125$  and from  $\tan(\beta l) = -1$ , we find  $l/\lambda = 0.375$ . If we choose the nearest location (i.e.,  $l = 0.125\lambda$ ) for the quarter-wave transformer design, then  $T = +1$ , and substituting this value into the  $Z_1$  expression above yields

$$Z_1 = (50) \frac{(40 + j30) + j50}{50 + j(40 + j30)} = (50) \frac{40 + j80}{20 + j40} = 100\Omega$$

which is a purely resistive impedance, as expected. Using this value of  $Z_1$ , we can now determine the characteristic impedance of the quarter-wave transformer inserted at a distance of  $l = 0.125\lambda$  away from the load to match the load impedance  $Z_L = 40 + j30\Omega$  to the  $Z_0 = 50\Omega$  line as

$$Z_Q = \sqrt{Z_0 Z_1} = \sqrt{(50)(100)} \simeq 70.7\Omega$$

(Note that if the other location was chosen for the design, then  $T = -1$ , and the input impedance of the  $50\Omega$  line at that location is  $Z_1 = 25\Omega$  and therefore for a quarter-wave transformer introduced at that position, the characteristic impedance would be  $Z_Q = \sqrt{(50)(25)} \simeq 35.4\Omega$ .)

(b) Following the same steps with  $Z_L = 80 - j60\Omega$ , we have

$$\begin{aligned} Z_1 &= (50) \frac{(80 - j60) + j50T}{50 + j(80 - j60)T} = (50) \frac{80 + j(50T - 60)}{(50 + 60T) + j80T} \\ &= (50) \frac{[80 + j(50T - 60)][(50 + 60T) - j80T]}{(50 + 60T)^2 + (80T)^2} \end{aligned}$$

Equating the imaginary part of  $Z_1$  to zero yields

$$\begin{aligned} \Im\{Z_1\} = 0 &\rightarrow (50T - 60)(50 + 60T) - (80)^2 T = 0 \\ &\rightarrow 6T^2 - 15T - 6 = 0 \rightarrow T \simeq 2.85, -0.351 \end{aligned}$$

From  $\tan(\beta l) \simeq 2.85$ , we find  $l/\lambda \simeq 0.196$  and from  $\tan(\beta l) \simeq -0.351$ , we find  $l/\lambda \simeq 0.446$ . Choosing  $l \simeq 0.196\lambda$  (i.e., the nearest location with respect to the position of the load) for the design, the value of  $Z_1$  at that position is

$$Z_1(l \simeq 0.196\lambda) \simeq (50) \frac{80(50 + 60T) + 80T(50T - 60)}{(50 + 60T)^2 + (80T)^2} \bigg|_{T \simeq 2.85} \simeq 18.1\Omega$$

To match  $Z_1 \simeq 18.1\Omega$  to  $50\Omega$ , we need a quarter-wave transformer with characteristic impedance given by

$$Z_Q = \sqrt{Z_0 Z_1} \simeq \sqrt{(50)(18.1)} \simeq 30.1\Omega$$